

Motaseem Billah Asik
221-15-4976
61-L

Device 1: Temperature Sensor:-

It helps monitoring temperature in crucial various industries.

Device-2: Keypad Controller Lock System:-

It is widely used in security applications.

Device-3: Digital clock with alarm:-

Realtime clock implementations are fundamental in embedded system.

Truth Table:- Temperature Sensor:-

Temperature (C)	ADC Input	Output (Binary)
0	0000	0000
10	0001	0001
20	0010	0010
30	0011	0011
40	0100	0100


Truth Table:- Keypad:-

Keypad input	Current state	Next state	Lock status
1	0000	0001	locked
2	0001	0010	locked
3	0010	0011	locked
4	0011	0100	unlocked
5	0100	0000	locked


Truth Table:-

Seconds	Reset	Q ₀	Q ₁	Q ₂	Q ₃
0	0	0	0	0	0
1	0	1	0	0	0
2	0	0	1	0	0
3	0	1	1	0	0
4	0	0	0	1	0

Temperature Diagram:-

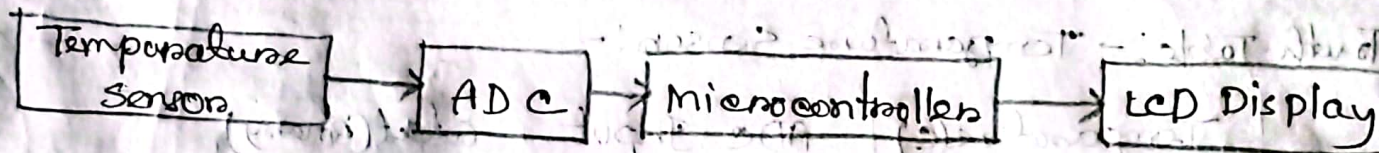

Keypad Diagram:-

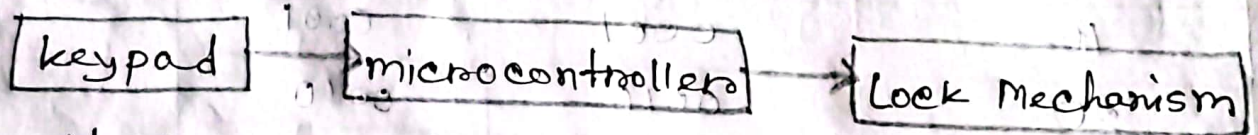

Circuit Diagram: Digital clock:-

